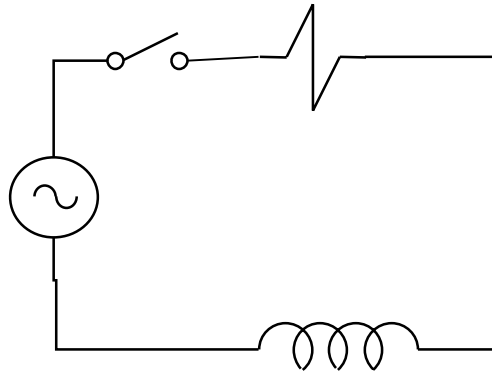


## Homework Exercise: Current-Limiting Circuit Breaker

Purpose of the exercise is to write a Matlab script to evaluate arc energy  $W_a$ , Joule integral  $I^2t$  and actual (limited) current peak in interruption of a resistive and inductive AC circuit by a limiting circuit breaker.



Supply voltage is:

$$e = E \cos(\omega t + \psi), \quad \frac{E}{\sqrt{2}} = 400V, \quad f = 50Hz.$$

Plot the total current " $i_{tot}$ ", as distorted by the arc voltage, assuming worst-case asymmetrical prospective current, in the case current is interrupted by a limiting breaker.

Determine arc energy, peak value of current and Joule integral. **Assume that no arc reignitions occur.**

Repeat calculations for different values of short circuit prospective currents  $I_{cc-pr}$  (consider values from 1 to 100kA RMS): plot  $I^2t$ , arc energy and peak current value as a function of the prospective RMS current. Always consider R and L so that *Power factor* = 0.2.

Data for the limiting breaker:

Contact separation at  $\bar{t} = 0,5 \text{ ms}$

Arc voltage: choose one of the two possibilities below:

a) constant value  $e_a = 350V$

b) linearly increasing arc voltage:

- for  $0,5 \text{ ms} \leq t \leq t_e$ :  $e_a = k_2 \cdot t$ , with  $k_2 = 250 \text{ V/ms}$  and  $t_e = 1.8 \text{ ms}$

- for  $t_e \leq t \leq t_f$ :  $e_a$  maintains a constant value

$t_f$  = instant of arc extinction

Optional:

*ELECTRICAL SWITCHING DEVICES – 2020-2021 - HOMEWORK*

Plot charts to compare values of  $I^2t$ , arc energy and peak current with those obtained with a non-limiting breaker, which interrupts current at first zero crossing.